Worked Solutions for ENGAA Papers by Topic

Section 1

Topic: Electricity

Section 1 Topic	Number of Questions 2016 - 2020
Algebra	34
Calculus	16
Coordinate geometry	11
Electricity	18
Energy	8
Exponentials and logarithms	9
Forces and equilibrium	
Geometry	40
Kinematics	15
Materials	2
Matter & thermal physics	5
Mechanics	55
Number	11
Probability	3
Radioactivity	14
Ratio and proportion	7
Sequences and series	8
Trigonometry	6
Waves	13

5 A dc electricity transmission system uses an undersea cable to send electricity from one country to another. On a particular day, the first country supplies electricity at a voltage of 400 kV and 2000 A to the transmission system. The second country receives electricity from the transmission system at 160 kV and 4000 A.

What is the percentage efficiency of the system and how much energy is wasted every minute?

	efficiency %	energy wasted every minute / J
Α	20	9.6×10^{9}
в	20	3.84 × 10 ¹⁰
С	20	4.8 × 10 ¹⁰
D	80	9.6×10^9
Е	80	$3.84\times\mathbf{10^{10}}$
F	80	4.8 × 10 ¹⁰

ENGAA S1 2020 - Question 5 - Worked Solution



7 Two fixed horizontal metal rails are side by side and 12 cm apart. The rails are connected to a dc power supply by a switch that is initially open.

A freely moveable metal rod of length 20 cm is placed on the rails as shown in the diagram. The diagram shows the arrangement seen from above.

The angle between the rod and the rails is 90°.



fixed rails

The whole arrangement is placed in a uniform magnetic field of magnitude 0.50 T that is directed perpendicularly into the page.

The moveable rod has a weight of 0.40 N.

The switch is now closed. As a result, there is a current of 2.4 A in the circuit and the rod moves.

What is the initial magnitude of the acceleration of the rod and what is its direction?

acceleration / m s⁻² direction Α 0.36 to the left в 0.36 to the right С 0.60 to the left D 0.60 to the right Е 3.6 to the left F 3.6 to the right G 6.0 to the left н 6.0 to the right

 $(gravitational field strength = 10 N kg^{-1})$

ENGAA S1 2020 - Question 7 - Worked Solution

 $a = \frac{BIl}{m}$ $a = 3.6ms^{-2}$ From left hand rule $F = I.B \times h$ Thus force to right

27 A flat rectangular coil of wire with sides of length 30 cm and 20 cm is freely pivoted about an axle. The axle passes through the middle of the sides of length 30 cm.

Part of the coil is between the poles of a U-shaped magnet as shown in the diagram. The poles are 4.0 cm long. The magnetic field can be considered uniform between the poles, and zero elsewhere.

The coil is connected to a power supply so that there is a current in it.



F = BIl J = F.d J = BIl.d $J = 0.05 \times 0.6 \times (4 \times 10^{-2} \times 50) \times 15$ J = 0.90Ncm

31 Electrical power is supplied through a dc transmission line that consists of two metal wires. Each wire is 8.0 km long and has a cross-sectional area of 1.0 cm².



The resistivity of the metal from which the wires are made is $2.5 \times 10^{-7} \Omega$ m.

Electrical power is transmitted to the transmission line at a potential difference of 24 000 V.

At what rate is energy being wasted as heat in the wires when the power supplied to the transmission line is 120 kW?

- A 0.40W
- **B** 0.80 W
- C 1.6W
- **D** 250 W
- E 500W
- F 1000 W
- G $1.44 \times 10^7 W$
- H 5.76 × 10⁷ W

ENGAA S1 2020 - Question 31 - Worked Solution

$$P = \frac{RA}{l} \rightarrow R = 40\Omega$$
$$P = IV \rightarrow I = 5A$$
$$P_{disjusted} = I^2 R = 1000W$$

Jadmission

39 In the following circuit, the ammeter records a current of zero.



ENGAA S1 2020 - Question 39 - Worked Solution

$$for I_0 = 0, v_1 = v_2$$

$$\frac{3000}{200 + 100} \cdot 6 = \frac{R}{1200 + R} \cdot 16$$

$$4(1200 + R) = 16R$$

$$12R = 4800\Omega$$

$$R = 400\Omega$$

Answer is D ENGAA S1 2019 - Question 2 2 The current-voltage graph for a diode is shown.



The diode is connected in series with a resistor and a 6.0 V battery. The current in the circuit is 8.0 mA.

What is the resistance of the resistor?

(Assume that the battery has negligible resistance.)

- **A** 0.15Ω
- **B** 0.60 Ω
- **C** 0.75Ω
- D 4.8Ω
- Е 150Ω
- F 600Ω
- **G** 750 Ω

ENGAA S1 2019 - Question 2 - Worked Solution

$$V = IR \quad \rightarrow R = \frac{V}{I}$$
$$I = 8mA$$

$$V = 1.2V$$

$$V_{res} = 6V - 1.2V = 4.8$$

$$R = \frac{4.8V}{8mA} = 600\Omega$$

8 The secondary coil of an ideal, 100% efficient transformer is connected to a resistor by cables of total resistance 1500Ω . The current in the primary coil is 4.0 A. There are 240 turns in the primary coil and 4800 turns in the secondary coil.

What is the power produced as heat in the cables?

- **A** 60 W
- **B** 300 W
- **C** 6000 W
- D 24000W
- E 120000W
- F 9600000W

ENGAA S1 2019 - Question 8 - Worked Solution



16 In the following circuit, all five resistors have the same resistance.



ENGAA S1 2019 - Question 16 - Worked Solution



26 A metal wire of length 0.50 m has a uniform cross-sectional area of 4.0×10^{-7} m².

There is a current of 4.0 A in the wire.

What is the potential difference across the ends of the wire?

(resistivity of the metal = $1.6 \times 10^{-7} \Omega m$)

- A 0.05V
- **B** 0.20V
- C 0.80V
- D 3.2V
- E 5.0V
- F 20V

ENGAA S1 2019 - Question 26 - Worked Solution

34 A student has one 300Ω resistor and another resistor of resistance R.

The student plots a graph of current *I* against potential difference *V* for the 300Ω resistor and then for both resistors connected in parallel.



ENGAA S1 2019 - Question 34 - Worked Solution

$$V = IR$$

$$R = \frac{V}{I}$$

$$\frac{6V}{30 \times 10^{-3}mA} = 200\Omega$$

$$R' = \left(\frac{1}{R} + \frac{1}{300}\right)$$

$$R' = 200\Omega = \left(\frac{1}{R} + \frac{1}{300}\right)$$
$$\frac{1}{R} = \frac{1}{200} - \frac{1}{300} = \frac{100}{60000}$$
$$R = 600\Omega$$



ENGAA Specimen S1 - Question 6

- 6 Which of the following is a correct unit of potential difference (voltage)?
 - A amp per ohm
 - B coulomb per joule
 - C joule per second
 - D newton per coulomb
 - E watt per amp

ENGAA Specimen S1 - Question 6 - Worked Solution

E = QV, V = IR, P = IVWrite out equations that use voltage Look at the units and see what correspond to possible answers. Answer is E

ENGAA Specimen S1 – Question 18

18 Two resistors with resistance R_1 ohms and R_2 ohms are connected in series with a battery that has a voltage V across its terminals.

Which formula gives the power dissipated by the resistor with resistance R_1 ohms?

$$\mathbf{A} \quad \frac{VR_1}{R_1 + R_2}$$
$$\mathbf{B} \quad \frac{V^2R_1}{R_1 + R_2}$$
$$\mathbf{C} \quad \frac{VR_1}{(R_1 + R_2)^2}$$
$$\mathbf{D} \quad \frac{V^2R_1}{(R_1 + R_2)^2}$$

$$\mathbf{E} \quad \frac{VR_1^2}{(R_1 + R_2)}$$
$$= \quad V^2R_1^2$$

$$\mathbf{F} = \frac{V^2 R_1^2}{(R_1 + R_2)^2}$$

ENGAA Specimen S1 - Question 18 - Worked Solution

$$R_T = R_1 + R_2$$

$$I = \frac{V}{R_T}$$

$$P_1 = I^2 R_1$$

$$P_1 = \frac{V^2}{(R_1 + R_2)^2} R_1$$

4 The diagram shows three resistors R₁, R₂ and R₃ connected in series with a battery of constant voltage. The resistance of each resistor and the corresponding current are also shown.



Resistor R₃ is now removed and the circuit is reconnected.

What is the new current in the circuit?

A 0.20A
B 0.22A
C 0.33A
D 0.40A
E 0.50A
F 2.0A
G 6.0A

ENGAA S1 2018 - Question 4 - Worked Solution

$$R_T = R_1 + R_2 + R_3 = 30\Omega$$
$$V = IR$$
$$= 0.2 \times 30$$
$$= 6$$

10 The potential difference across the motor in an electric car is 400 V and the current in the motor is 1250 A.

The car accelerates along a horizontal road from rest for 4.0 s.

The efficiency of the overall system is 45%.

What is the kinetic energy of the car at the end of the 4.0 s?

(Ignore energy losses due to air resistance and due to friction between the tyres and the road.)

- A 225000 J
- **B** 500000J
- C 900000J
- D 1250000 J
- E 2000000J

ENGAA S1 2018 - Question 10 - Worked Solution



Answer is C.

26 The diagram shows a circuit containing a battery and three identical resistors X, Y and Z.



The total power supplied by the battery is 18 W.

What is the power dissipated as heat in resistor X?

- A 1.5WB 2.0W
- **c** 3.0 W
- **D** 4.5W
- **E** 6.0 W
- **F** 8.0 W
- **G** 12W

26 Wet

ENGAA S1 2018 - Question 26 - Worked Solution

$$R_T = \left(\frac{1}{R} + \frac{1}{R}\right)^{-1} + R$$
$$= \frac{R}{2} + R$$
$$= \frac{3R}{2}$$
$$P = I^2 R$$
$$= \frac{I^2 \times 3R}{2} = 18$$
$$I^2 R = 12$$
X and Y have same V and R
$$I_1 = I_2$$
$$I = I_1 + I_2$$

 $I_{1} = \frac{I}{2}$ So power dissipated in X is: $P_{x} = RI_{1}^{2}$ $= \frac{I^{2}}{4}R$ $= \frac{12}{4}$ = 3W

Answer is C.



20 A kettle is designed to work from a car's power socket. The kettle has a power rating of 150 W when a constant voltage of 12.0 V d.c. is applied across its element.

How much charge passes through the element of this kettle when the voltage of 12.0 V is applied across it for 20 minutes?

- A 96 C
- **B** 250 C
- **C** 15000 C
- D 36000 C
- E 900 000 C
- F 2160000C

ENGAA 2017 - Question 20 - Worked Solution



8 A circuit consists of a 5.0 Ω resistor and a variable resistor connected in series with a 24 V battery. The variable resistor has a minimum resistance of 3.0 Ω and a maximum resistance of 15 Ω. The battery and the connecting wires have negligible resistance.

What is the maximum power dissipated in the 5.0Ω resistor?

- **A** 7.2W
- **B** 18W
- C 27 W
- **D** 45W
- E 72W
- F 75W

ENGAA S1 2016 - Question 8 - Worked Solution



For the maximum power in the 5.0 Ω resistor, find the maximum voltage across it By Kirchoff's voltage law the sum of voltages across the resistors will be 24V

$$V_i = V_{in} \frac{R_i}{R_T}$$

For maximum voltage across 5Ω resistor, $\frac{5}{R_T}$ must be maximum so the variable resistor must have the minimum resistance

$$V_1 = 24 \times \frac{5}{8} = 15V$$
$$P = \frac{V^2}{R} = 45W$$

16 A heater is connected in series with a resistor and a 6.0 V battery in the circuit shown.



The total resistance of the circuit is 15Ω . In 3.0 minutes, 180 J of electrical energy is transferred into other forms in the heater.

How much charge flows through the heater in the 3.0 minutes and what is the voltage across the heater?

	charge / C	voltage / V			
Α	1.2	150			
в	1.2	276	5		
С	7.5	0.041 gNCEL			
D	7.5	24			
Е	72	0.40			
F	72	2.5			
G	450	0.40			
н	450	2.5			

ENGAA S1 2016 - Question 16 - Worked Solution

The heater is R₁

$$P = \frac{V^2}{R} = \frac{\Delta E}{\Delta t}$$



